



North South University
Department of Electrical & Computer Engineering

LAB REPORT

Course Name: **CSE332L- Computer Organization and Architecture Lab**

Experiment Number: 05

Experiment Name: Design of a register file

Experiment Date: 21.11.21

Report Submission Date: 21.11.21

Section: 07

Group Number:

Student Name: Riaz Mehadi	Score
Student ID: 1931746042	
Remarks:	

Exp Name: Design of a register file

Objectives:

We will have following objectives to fulfill:

- 1) Design a register file that is 16 bit wide. Label properly the inputs/outputs/selections .
- 2) Design the interfacing for reading data from any of those registers.
- 3) Design the interfacing for writing data to any of those registers. Make sure it has the write control signal.

Circuit Diagrams:

Discussion:

In this experiment, I gather knowledge about design of a register file. Firstly, I take D-mux which has write enable and RD is the part of register. Then, I take 16 register which is connected by enable pin with D-mux. In register, there is two more button for reset and clock. Then I take two mux for reading data 1 and 2 and two selector RS and RT which is mainly the part of register.

Then I take another file. Then I take a Rom and register for controlling the register read and write which consist of OP, RS, RT, RD. Then I take the ic of register file. Then I connect everything like RS, RT, RD. After that I take the ic of 16 bit Alu from my project then I connect the result of Alu with the data input of register file which is used for writing. By the help of clock plus, I can write the data in register file.

During the experiment, I face a problem, like my circuit output is showing wrong output. By the help of my lab instructor, I solve the problem. Then I do all things successfully.