



North South University
Department of Electrical & Computer Engineering

LAB REPORT

Course Name: **CSE332L- Computer Organization and Architecture Lab**

Experiment Number:

Experiment Name: Design a 4-bit Binary Multiplier

Experiment Date: 31.10.21

Report Submission Date: 31.10.21

Section: 7

Group Number:

Student Name: Riaz Mehadi	Score
Student ID: 1931746042	
Remarks:	

Exp: Design a 4-bit Multiplier


Objectives:



1. Understanding behavior of combinational multiplier from module designed by the student as part of the experiment.
2. Understanding the theory and implement the multiplication unit which is as follows (along with the logic diagram below).
3. Check Multiplying bits and Show the sum outputs.

Apparatus:

1. 4 X 7408 AND IC .
2. 3X 7483 or 74283 4-bit Adder IC .
3. Trainer Board □ Wires.

LOGIC CIRCUIT DIAGRAM

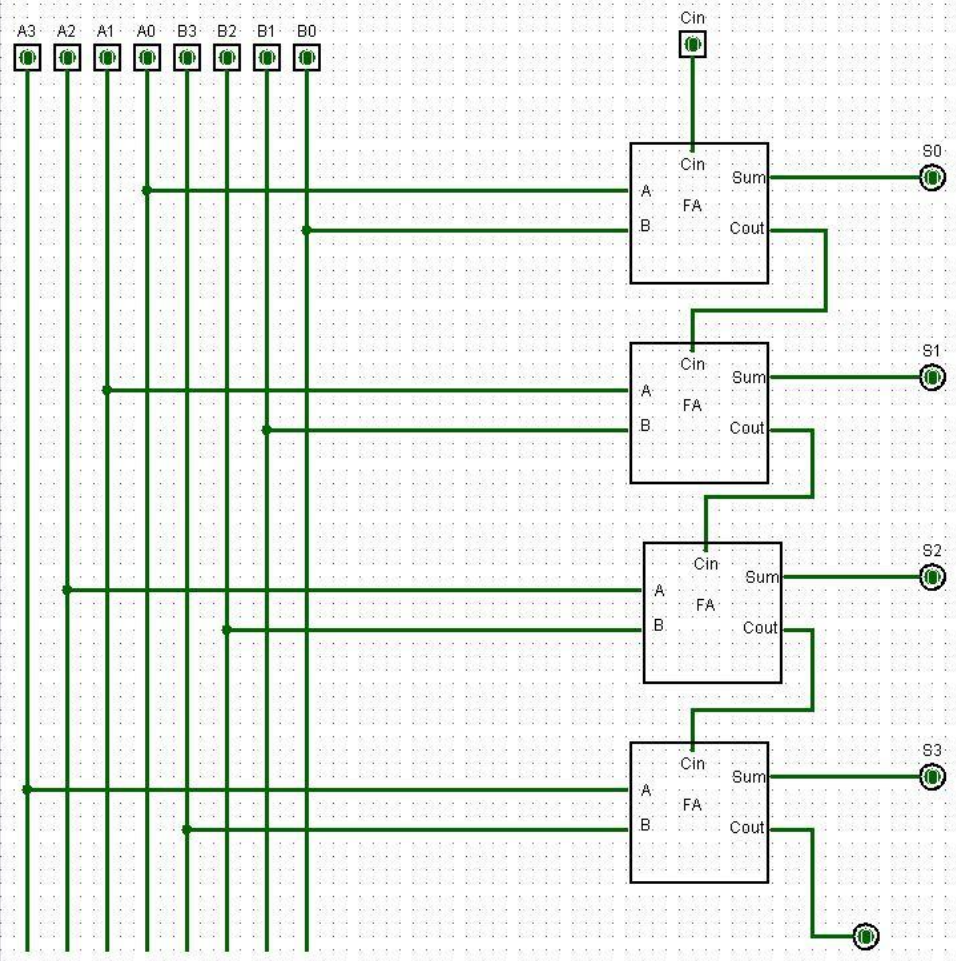

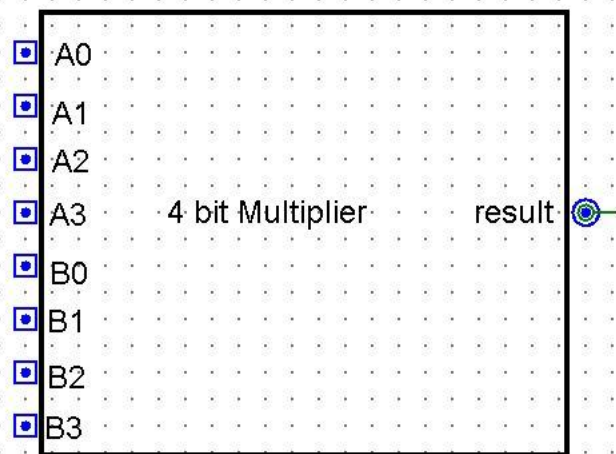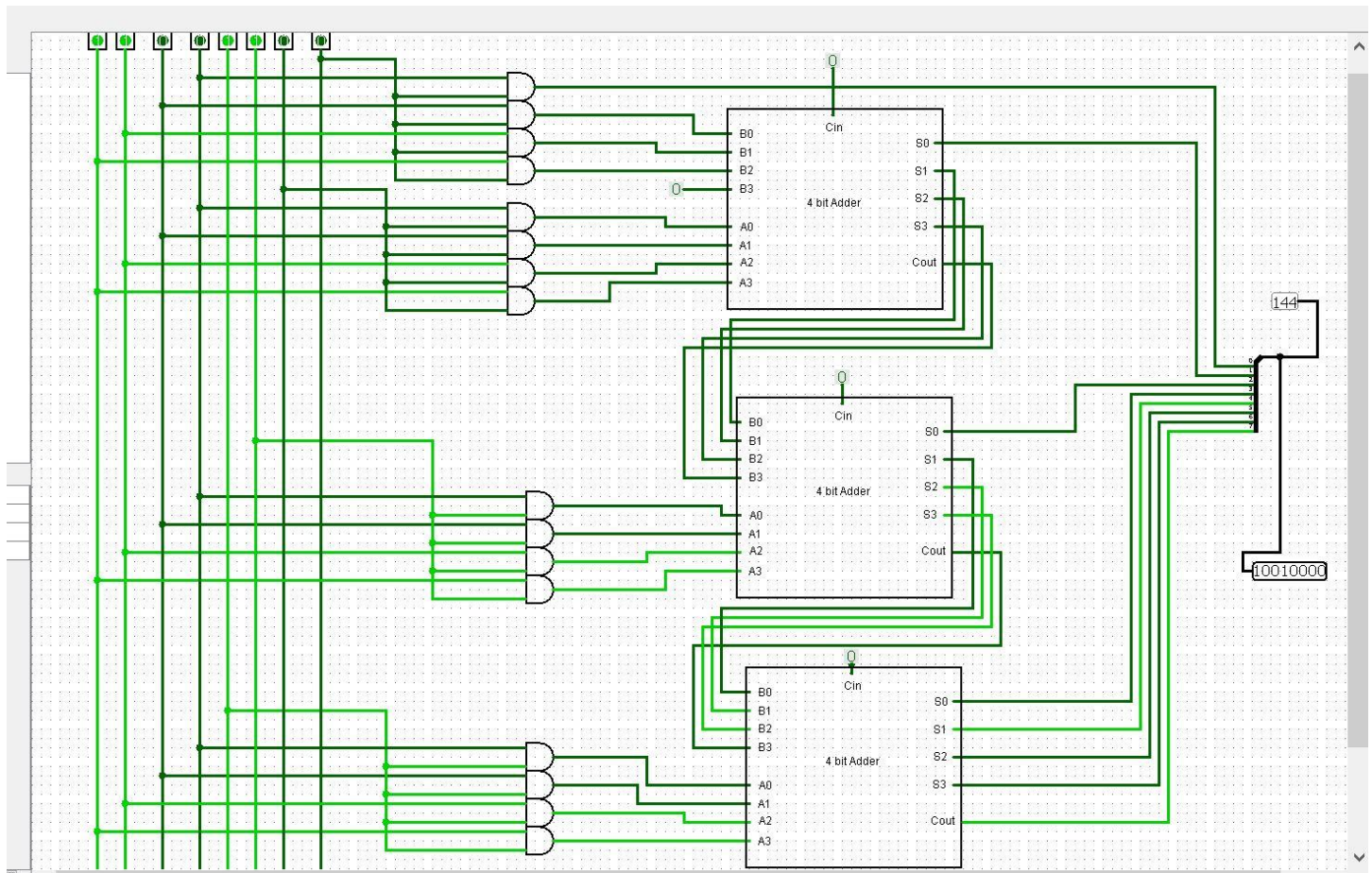

Data Table:1 Theoretical

Multiplicand	Multiplier	Product	Result in Decimal
A4 A3 A2 A1	B4 B3 B2 B1	S8 S7 S6 S5 S4 S3 S2 S1	

1 0 0 0	1 0 0 1	0 1 0 0 1 0 0 0	8 × 9 = 72
0 1 0 1	0 0 1 0	0 0 0 0 1 0 1 0	5 x 2 = 10
0 1 1 1	0 0 1 1	0 0 0 1 0 1 0 1	7 x 3 = 21
0 1 0 0	1 0 0 0	0 0 1 0 0 0 0 0	4 x 8 = 32
0 1 0 1	0 1 1 0	0 0 0 1 1 1 1 0	5 x 6 = 30
1 0 0 1	0 1 0 0	0 0 1 0 0 1 0 0	9 x 4 = 36
1 1 1 1	1 0 1 1	1 0 1 0 0 1 0 1	15 x 11 = 165

Data Table:2 Experimental

Multiplicand A4 A3 A2 A1	Multiplier B4 B3 B2 B1	Product S8 S7 S6 S5 S4 S3 S2 S1	Result in Decimal
1 0 0 0	1 0 0 1	0 1 0 0 1 0 0 0	8 × 9 = 72
0 1 0 1	0 0 1 0	0 0 0 0 1 0 1 0	5 x 2 = 10
0 1 1 1	0 0 1 1	0 0 0 1 0 1 0 1	7 x 3 = 21
0 1 0 0	1 0 0 0	0 0 1 0 0 0 0 0	4 x 8 = 32
0 1 0 1	0 1 1 0	0 0 0 1 1 1 1 0	5 x 6 = 30
1 0 0 1	0 1 0 0	0 0 1 0 0 1 0 0	9 x 4 = 36
1 1 1 1	1 0 1 1	1 0 1 0 0 1 0 1	15 x 11 = 165

Discussion:

In this experiment, I gathered knowledge about 4 bit Binary Multiplier. For implementing 4 bit Binary Multiplier, I had to use 4 bit adder, some AND gate for taking input which is output of AND gate. Firstly, I made 1 bit adder. By using 1 bit adder's IC, I made 4 bit adder. I also use

And,OR,X-OR gate for makingAdder.I learn how to make a ic by our own circit .It is very helpful but I do not have to make same circuit again and again.I also learn how to make 4 or more bit logic unit by using 1 or more bit ic.

For making 4 bit BinaryMultiplier,I use three 4 bit adder's ic.Firstly,I take one copy of 4 bit ic from adder's ic .Then I take rest of the two ic in the same process.I use splitter for showing the output of BinaryMultiplier.One splitter use for showing binary output and I use same splitter for showing output in decimal form by the help of probe.This part was very interesting for me.

During the experiment,I face a problem,like my circuit output is showing wrong output .By the help of my lab instructor ,I solve the problem.Then I do the all thing successfully.