

**North South University**  
Department of Electrical & Computer Engineering

**LAB REPORT**

Course Name: **CSE332L- Computer Organization and Architecture Lab**

Experiment Number: 02

|   |
|---|
| Experiment Name: Design of a 4 bit logic unit |
|---|

Experiment Date: 24.10.21

Report Submission Date: 24.10.21

Section: 07

Group Number:

|                           |       |
|---------------------------|-------|
| Student Name: Riaz Mehadi | Score |
| Student ID: 1931746042    |       |
| Remarks:                  |       |

## **Exp: Lab 02 – Design a 4 Bit Arithmetic Unit**

### **Objectives:**

1. 1 -bit full Adder
2. 1-bit Arithmetic Unit 3.
3. 4 - bit AU with ( Addition, SUBtraction, transfer, Inc, Dec)



### **Equipment List:**

1. Trainer board.
2. IC 7404, 7483 or 74283, 74LS153.
3. wires for connection.


**Data Table:**

| S1 | S0 | Cin | A3 | A2 | A1 | A0 | B3 | B2 | B1 | B0 | Cout | D3 | D2 | D1 | D0 | Micro operation      |
|----|----|-----|----|----|----|----|----|----|----|----|------|----|----|----|----|----------------------|
| 0  | 0  | 0   | 0  | 0  | 0  | 1  | 0  | 0  | 0  | 1  | 0    | 0  | 0  | 1  | 0  | Add                  |
| 0  | 0  | 1   | 0  | 0  | 1  | 1  | 0  | 1  | 0  | 0  | 0    | 1  | 0  | 0  | 0  | Add with Carry       |
| 0  | 1  | 0   | 0  | 0  | 1  | 0  | 1  | 1  | 0  | 0  | 0    | 0  | 1  | 0  | 1  | Subtract with Borrow |
| 0  | 1  | 1   | 0  | 1  | 1  | 1  | 0  | 1  | 0  | 0  | 1    | 0  | 0  | 1  | 1  | Subtract             |
| 1  | 0  | 0   | 1  | 0  | 1  | 1  | 0  | 1  | 0  | 0  | 0    | 1  | 0  | 1  | 1  | Transfer A           |
| 1  | 0  | 1   | 0  | 1  | 0  | 0  | 0  | 0  | 0  | 0  | 0    | 0  | 1  | 0  | 1  | Increment A          |
| 1  | 1  | 0   | 1  | 0  | 1  | 0  | 1  | 0  | 0  | 0  | 1    | 1  | 0  | 0  | 1  | Decrement A          |
| 1  | 1  | 1   | 1  | 0  | 0  | 1  | 0  | 1  | 1  | 1  | 1    | 1  | 0  | 0  | 1  | Transfer A           |


**Logic Circuit Diagram:**

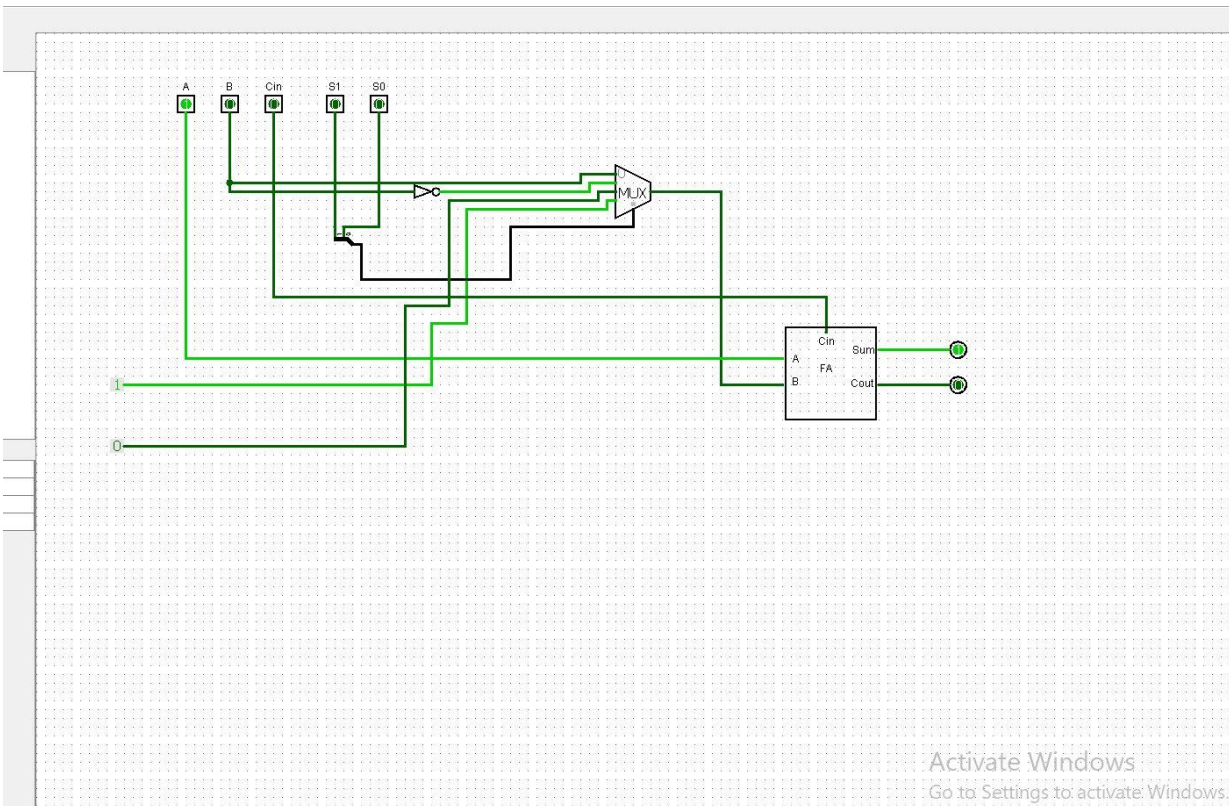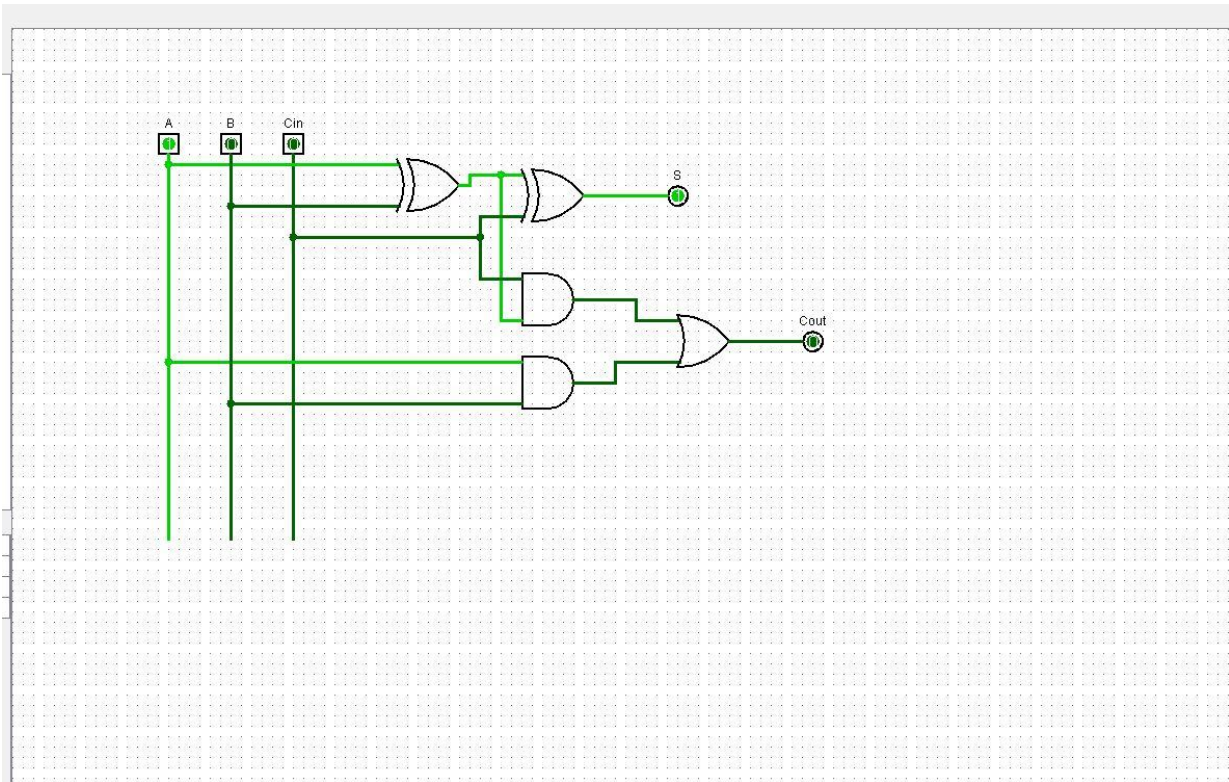

Activate Windows  
Go to Settings to activate Windows.

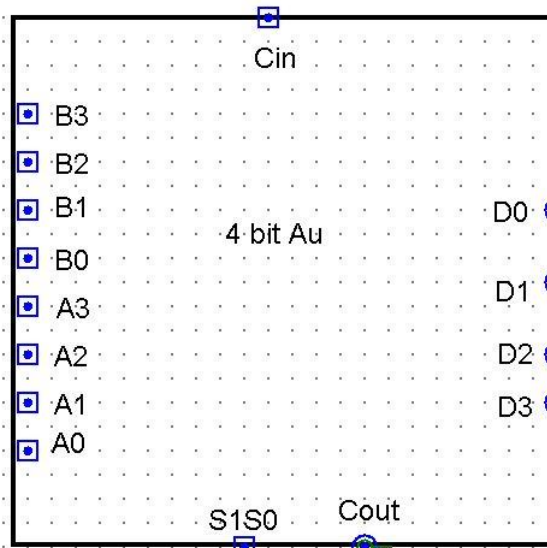

Activate V

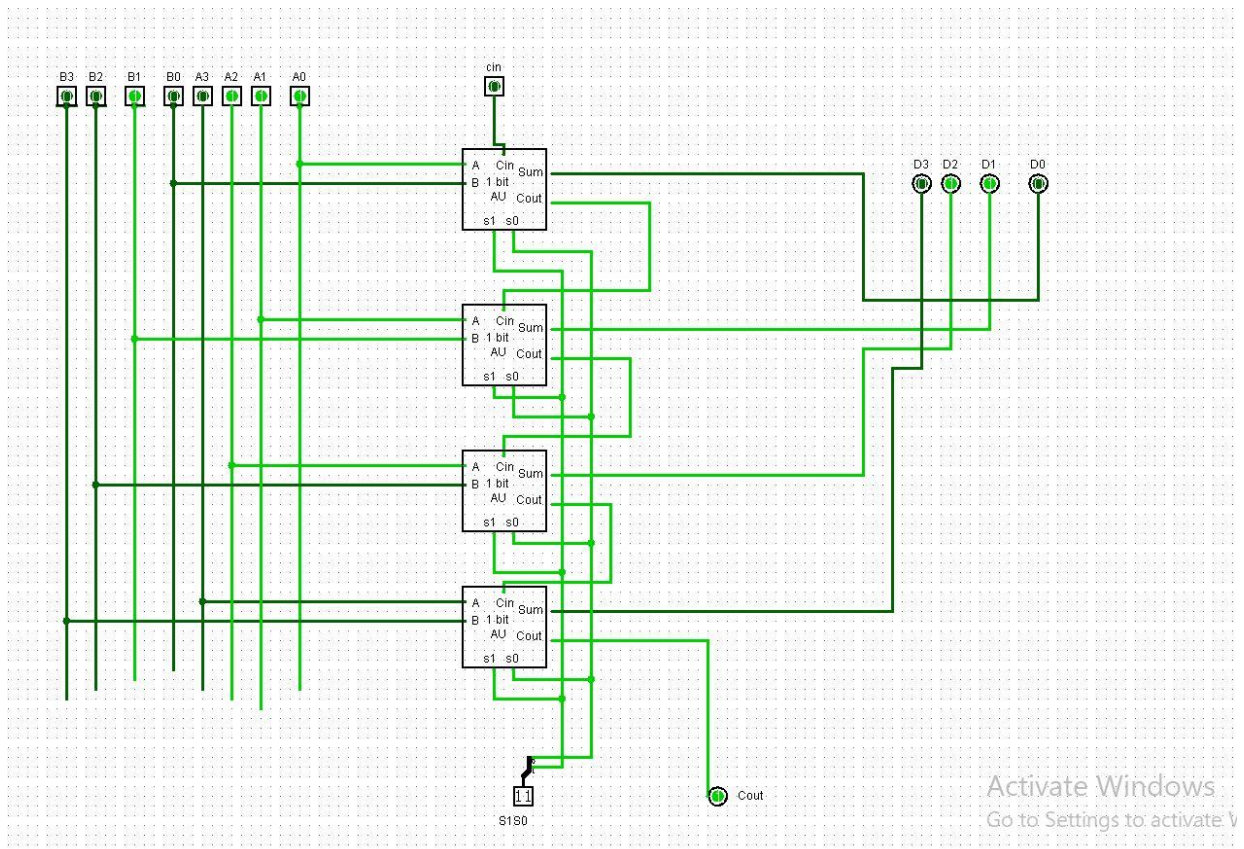

## Discussion:

In this experiment, I gathered knowledge about 1-bit and 4-bit Arithmetic Logic Units. Firstly, I made a 1-bit logic unit, which is comparatively easier than a 4-bit Arithmetic Logic Unit. I also gathered knowledge about multiplexers, which I used for making an Arithmetic Logic Unit. I also used AND, OR, and X-OR gates for making an adder. I learned how to make a circuit by my own circuit. It is very helpful, but I do not have to make the same circuit again and again. I also learned how to make a 4-bit or more bit logic unit by using 1-bit or more bit ICs.

For making a 4-bit Arithmetic Logic Unit, I used four 1-bit Arithmetic Logic Unit ICs. Firstly, I took one copy of a 1-bit IC from a 1-bit Arithmetic Logic Unit IC's part. Then I took the rest of the three 1-bit ICs in the same process. I used two splitters for taking the input of the 4 ICs' input. One splitter was used for taking the input of A, and another one was used for taking the input of B. I used a 2-bit selector for selecting which gates' output I wanted to show. This part was very interesting for me.

During the experiment, I face a problem, like my circuit output is showing wrong output. By the help of my lab instructor, I solve the problem. Then I do the all thing successfully.